

University of Illinois at Urbana-Champaign

ECE 385

LAB 5

LAB REPORT

by Shubham Gupta & Devul Nahar (sg49 & danahar2)

3/20/2022

Introduction:

A processor has three essential components: the CPU, the memory that stores instructions and data, as well as an interface that allows communication between input/output devices. In this experiment, we will construct a 16-bit CPU in system Verilog known as the SLC3 (a subset of the LC3 ISA). The CPU oversees running the machine instruction cycle, which includes fetching data and instructions from the memory, decoding it in the control unit, and then executing it in the arithmetic/logic unit.

In particular, the CPU consists of a program counter register (PC), an instruction registers (IR), memory address register (MAR), a memory data register (MDR), an Instruction decoder, a status register (NZP), an 8x16 wide register file, and an arithmetic logic unit (ALU). PC stores the address of the next instruction to be executed. IR stores the address of the current instruction that is being executed. MAR stores the address of the memory block in which we want to read/write. MDR stores or the data to be written in or data read from the memory location pointed by MAR. The instruction decoder is responsible for decoding the 16-bit instruction into several parts such as opcode and its corresponding parts. The status register is responsible for adding conditional functionality into the SLC3. Register file holds 8 registers, each 16 bits wide. The register file is used to quickly access and store data. Finally, the ALU deals with arithmetic as well as logical operations responsible for manipulating data.

We implemented the entirety of this cycle in two parts. In the first week, we implemented the FETCH phase, in which we learned about the memory system as well as how memory interacts with the CPU. In addition, we dealt with CPU entities such as the ISDU control unit as well as built a basic data path to show the working of the FETCH phase. In the second week, we

implemented the DECODE and the EXECUTE phases of all the instructions in the SLC3 ISA.

We had to configure all the necessary state transitions as well as the inputs/outputs of each state.

Written Description and Diagram for SLC-3:

- a. **Summary of operation:** We first reset the machine by pressing CONTINUE and RUN together (note that both buttons are active low). To operate our SLC-3, we need to set the starting address of our instructions. To do this, we must set the address on the switches by hand that are present on the FPGA. Then to initialize it to the starting address we should push down the RUN key. Upon doing so we have initialized our SLC-3 and it is ready to execute the program. For example, to run I/O test 1, we set the switches to x0003. The push the RUN button. Now we can see that the program is running, whatever value we enter on the switches is displayed on the Hex Display. Similarly for programs that have a wait state, for example, I/O test 2, we must additionally press CONTINUE key to continue the execution of the process.

- b. **Description of SLC-3 functions:**

For any instruction to be carried out, we need to first FETCH the instruction from the memory. The FETCH itself has 3 states that must be carried out. The states are managed by the ISDU.sv, we start from state 18 where we set control signals to set MAR to PC and PC to PC + 1. Next, we go to state 33, which basically reads data from memory at MAR and updates MDR. This is a 3-state process as we wait for the memory to finish its task of reading data. Now we go to state 35, where we set control signals to set IR to MDR. At this point we have finished the FETCH part. We DECODE our instruction in state 32 as it is present in IR. Here we set control signals such that we can update BEN. This is done by bit-slicing IR register and if statements in our code. We also

get our Opcodes from IR [15:12] bits. The heart of our processor is the case statement. We use it to decide which state to enter next based on the extracted Opcode (implemented in ISDU.sv). This is the end of our DECODE. For the EXECUTE part, we have implemented the multi-state tree based on which the control signals are set to carry out various operations. In the last state of every operation, we always go back to state 18. This is how we ensure the cycle is complete.

The various functions our SLC-3 can perform are: Add, And, Not, Load, Store, Jump and Branch. We can perform two versions of ADD, the first one simply adds the value of source register 1 and source register 2, and updates the destination register with the sum. The second adds the content of source register to the sign extended value of the next 5 bits (immediate 5) and stores it to the destination register. We can perform two versions of AND, the first one simply ands the value of source register 1 and source register 2, and updates the destination register with the answer. The second ands the content of source register to the sign extended value of the next 5 bits (immediate 5) and stores it to the destination register. The NOT instruction simply negates the value of the source register and updates the destination register with the answer. We can conditionally choose to branch in our code, this is implemented by the BR operation. This is implemented by checking if any of the condition codes stored in the status register match the condition then a branch is taken. To do this, we simply update the PC to PC + sign extended value of the 9-bit offset provided in the instruction. We have two versions of jump statement, JMP and JSR. JMP simply copies the value of base register to the PC to perform an unconditional jump. Meanwhile JSR is used to jump to subroutines. Therefore, before performing the jump, we store the value of PC to register 7, and then

update the PC to $PC + \text{sign extended value of offset of 11 bits provided in the instruction.}$

By Load (LDR) operation we can simply load the value of memory stored at base register

+ an sign extended offset of 6 bits provided in the instruction, to the destination register.

Similarly, we have a store statement that stores the content of the source register at the

memory index base register + sign extended offset of 6 bits provided in the instruction.

The status registers are also updated upon the execution of ADD, AND, NOT, and LDR.

Instruction	Instruction(15 downto 0)							Operation
ADD	0001	DR	SR1	0	00	SR2	$R(DR) \leftarrow R(SR1) + R(SR2)$	
ADDi	0001	DR	SR	1	imm5		$R(DR) \leftarrow R(SR) + \text{SEXT}(\text{imm5})$	
AND	0101	DR	SR1	0	00	SR2	$R(DR) \leftarrow R(SR1) \text{ AND } R(SR2)$	
ANDi	0101	DR	SR	1	imm5		$R(DR) \leftarrow R(SR) \text{ AND } \text{SEXT}(\text{imm5})$	
NOT	1001	DR	SR	111111			$R(DR) \leftarrow \text{NOT } R(SR)$	
BR	0000	n	z	p	PCOffset9			if ((nzp AND NZP) != 0) $PC \leftarrow PC + \text{SEXT}(\text{PCOffset9})$
JMP	1100	000		BaseR	000000			$PC \leftarrow R(\text{BaseR})$
JSR	0100	1	PCOffset11				$R(7) \leftarrow PC;$ $PC \leftarrow PC + \text{SEXT}(\text{PCOffset11})$	
LDR	0110	DR	BaseR	offset6			$R(DR) \leftarrow M[R(\text{BaseR}) + \text{SEXT}(\text{offset6})]$	
STR	0111	SR	BaseR	offset6			$M[R(\text{BaseR}) + \text{SEXT}(\text{offset6})] \leftarrow R(SR)$	
PAUSE	1101	ledVect12						$LEDs \leftarrow \text{ledVect12}; \text{ Wait on Continue}$

Figure 1. SLC-3 Opcodes

c. Block Diagram:

 


Figure 2. Block Diagram

d. Description of .SV modules:

i. Module: Reg1.sv

Inputs: Clk, Reset, Load, D

Outputs: Data_Out

Description: It is the implementation of 1-bit register using always_ff.

Purpose: It is used in various places in the data path to store 1 bit data, for example, in BEN register.

 


Figure 3. Reg1.sv

ii. **Module:** Reg3.sv

Inputs: Clk, Reset, Load, [2:0] D

Outputs: [2:0] Data_Out

Description: It is the implementation of 3-bit register using always_ff.

Purpose: It is used in various places in the data path to store 3-bit data, for example, in NZP register.

 


Figure 4. Reg3.sv

iii. **Module:** Reg16.sv

Inputs: Clk, Reset, Load, [15:0] D

Outputs: [15:0] Data_Out

Description: It is the implementation of 3-bit register using always_ff.

Purpose: It is used in various places in the data path to store 3-bit data, for example, in PC register.

 


Figure 5. Reg16.sv

iv. **Module:** Mem2IO.sv

Inputs: Clk, Reset, [15:0] ADDR, OE, WE, [9:0] Switches, [15:0]

Data_from_CPU, [15:0] Data_from_SRAM

Outputs: [15:0] Data_to_CPU, [15:0] Data_to_SRAM, [3:0] HEX0, [3:0] HEX1, [3:0] HEX2, [3:0] HEX3

Description: It is used to implement memory mapped IO in our design. Load data from switches when address is xffff, and from SRAM otherwise. Implemented using if statement.

Purpose: It is crucial as it maps reading and writing to xffff to the LEDs and Switches respectively.

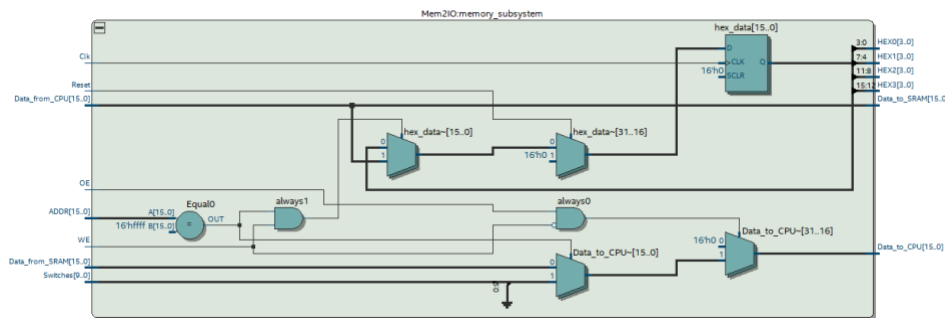


Figure 6. Mem2IO.sv

v. **Module:** HexDriver.sv

Inputs: [3:0] In0

Outputs: [6:0] Out0

Description: We use a UNIQUE switch case to map the binary values to the hexadecimal display. Given to us from previous labs.

Purpose: It maps the binary values to the hexadecimal LED display. Used for displaying values stored in registers. For user interface on the FPGA.

vi. **Module:** Datapath.sv

Inputs: LD_MAR, LD_MDR, LD_IR, LD_BEN, LD_CC, LD_REG, LD_PC, LD_LED, GatePC, GateMDR, GateALU, GateMARMUX, [1:0] PCMUX, [1:0] ALUK, [1:0] DRMUX, [1:0] SR1MUX, [1:0] SR2MUX, [1:0] ADDR1MUX, [1:0] ADDR2MUX, Mem_OE, Mem_WE, MIO_EN, Reset, Clk, [15:0] MDR_In

Outputs: [15:0] IR, MAR, MDR, BEN

Description: It holds all the components of our SLC-3 and connects the inputs and outputs. It holds all gates, selection MUXes, registers, ALU, and the data bus. We have implemented gates using if/case statements. Registers are updated conditionally based on control signals by case statements.

Purpose: It is the heart of our SLC-3 implementation. It receives signals from the ISDU and connects them to all the gates and MUXes to perform operations.

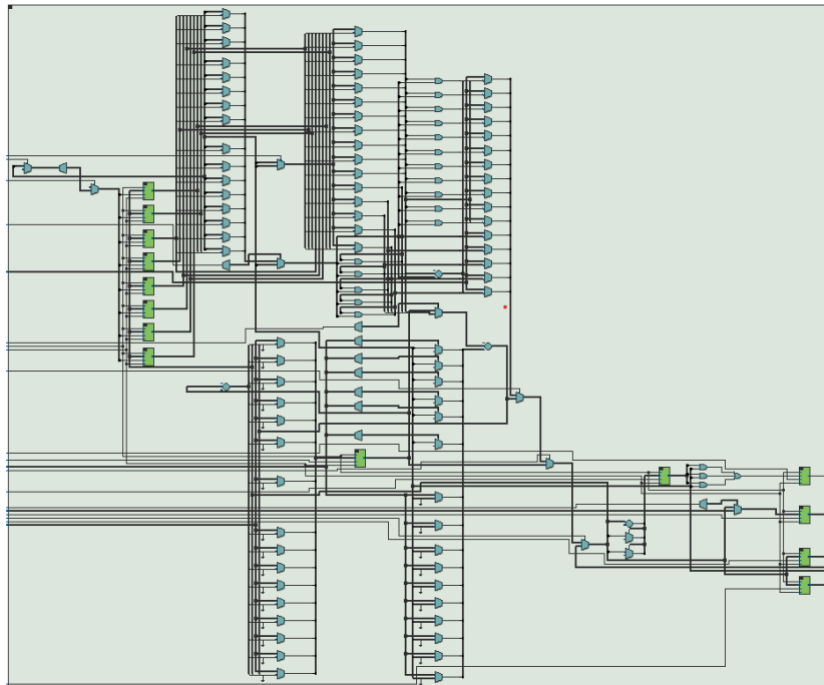


Figure 7. datapath.sv

vii. **Module:** ram.v

Inputs: [9:0] address, clock, [15:0] data, rden, wren

Outputs: [15:0] q

Description: It is an IP generated by Quartus, to implement the ram on board the FPGA.

Purpose: This module implements the RAM functionality on the SRAM present on the FPGA.

viii. **Module:** slc3.sv

Inputs: [9:0] SW, Clk, Reset, Run, Continue, [9:0] LED, [15:0]


Data_from_SRAM

Outputs: OE, WE, [6:0] HEX0, HEX1, HEX2, HEX3, [15:0] ADDR, [15:0]

Data_to_SRAM

Description: We initialize the instances of Mem2IO, data path and ISDU. We also create instances of hex drivers for the hex display here.

 Purpose: It is the top-level entity of our on-board design. It connects the inputs and outputs of data path, ISDU and Mem2IO. Also connects the hex displays.



e. State Diagram of ISDU:

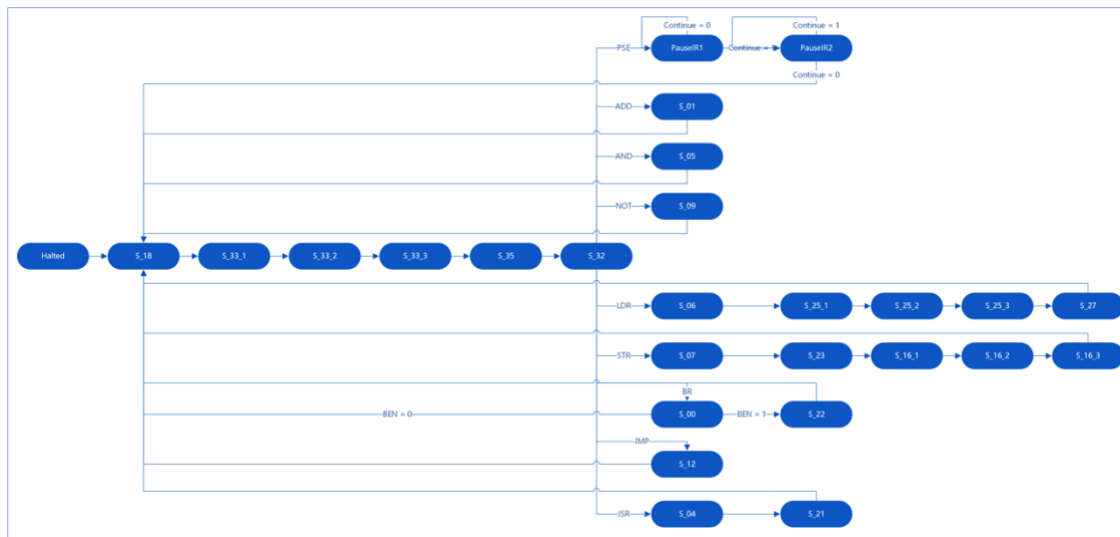


Figure 8. State Diagram of ISDU

Simulations of SLC-3 Instructions:

To decode what is on the HEX displays use the following table:

Hex Display Binary Code	Hex Equivalent
1000000	0
1111001	1
0100100	2
0110000	3
0011001	4
0010010	5
0000010	6
1111000	7
0000000	8
0010000	9
0001000	A
0000011	B
1000110	C
0100001	D
0000110	E
0001110	F

PauseIR state to press continue before displaying the contents of the switches on the Hex Display. We can see exactly this behavior represented in the simulation. Though x2 is put on switches, the value of the switches doesn't change until the continue button is pressed. Similar behavior occurs when x3 is put on switches.

Self-Modifying Test:



Figure 11. Self-Modifying Test

Before we execute the test, we first reset the machine by pressing continue and run together (note that both buttons are active low). Now, the third test resides at the memory location xB, so xB is put in the switches and run is pressed so that PC starts executing instructions from that memory address. This test uses a similar loop as the last program, however, the data for each pause instruction is incremented by one each time the person presses continue. As you can see from the simulation, the machine remains in the PauseIR state until continue is pressed, and when continue has pressed the value of LED is incremented by 1 (shown in red). This happens each time continue is pressed and the machine is in the PauseIR state.

XOR Test:

 


Figure 12. XOR Test

Before we execute the test, we first reset the machine by pressing continue and run together (note that both buttons are active low). Now, the fourth test resides at the memory location x14, so x14 is put in the switches and run is pressed so that PC starts executing instructions from that memory address. In this test, I am going to be XORing x2 and x1 together to get an output of x3. To do this, I first push x2 into the switches and then press continue (while the machine is in the PauseIR state). Similarly, I put x1 into switches and press continue. Finally, I get output of x3 in the HEX displays as I was expecting.

Multiplier Test:

 


Figure 13. Multiplier Test

Before we execute the test, we first reset the machine by pressing continue and run together (note that both buttons are active low). Now, the fifth test resides at the memory location x31, so x31 is put in the switches and run is pressed so that PC starts executing instructions from that memory address. In this test, I am going to be multiplying x2 and x1 together to get an output of x2. To do this, I first push x2 into the switches and then press continue (while the machine is in the PauseIR state). Similarly, I put x1 into switches and press continue. Finally, I get output of x2 in the HEX displays as I was expecting.

Sort Test:

 


Figure 15. Sort Test part 1



Figure 14. Sort Test part 2

Before we execute the test, we first reset the machine by pressing continue and run together (note that both buttons are active low). Now, the sixth test resides at the memory location x5a, so x5a is put in the switches and run is pressed so that PC starts executing instructions from that memory address. Once this is done, the user must decide between 1 of 3 modes: 1) Entering x0001 will call the “data entry” function (which will allow the user to put in any values the user wants inside the memory), entering x0002 will call the “sort” function (sorts whatever data is present in the memory contents), and entering x0003 will call the “display” function (will display all the values inside the memory). We first want to see, the contents of memory and therefore we put x3 on switches and press continue. After some clock cycles, we see the first element of memory appear on the HEX display. Now, every time we press continue, we see the next element on memory. Note that x01 (the smallest element) is in the third position while xfa (the largest element) is in the fourth position. We can sort the memory contents by putting x2 on the switches and then pressing continue. To see sorted memory elements, we again put x1 on switches and press continue. Once we do that, we can see that x1 ends up as the first element of memory, while xfa becomes the last element on the list.

Post-Lab Questions:

LUT	821
DSP	0
Memory (BRAM)	18432
Flip-Flop	258
Frequency	64.62 MHz
Static Power	90 mW
Dynamic Power	10.81 mW
Total Power	112.15 mW

Our design for both weeks was fully functional. However, we had two major problems while we were trying to debug week 2 of the lab. Firstly, we noticed that in quite a few places we had forgotten to set LD.REG for register file to high whenever we were trying to set a particular register to some value. The other mistake we did was using one always comb block for the entire data path. This was quite difficult to debug as in theory it should have worked as everything in the always_comb is supposed to have sequentially.

What is MEM2IO used for, i.e., what is its main function?

Mem2IO provides us the functionality of memory mapped I/O in our SLC-3 design. The basic functionality is to provide a memory address to our CPU that are physical peripherals to our design like LEDs, switches etc. So, whenever CPU reads or writes to the special memory addresses, Mem2IO makes sure that the data is being read or written from switches or LEDs respectively.

What is the difference between BR and JMP instructions?

In a BR statement, first we check BEN, if it is 1 then we set PC to PC + offset9 (PC is updated with an offset).

In a JMP statement, we unconditionally set PC to whatever value is stored in the given base register. No offset.

What is the purpose of the R signal in Patt and Patel? How do we compensate for the lack of the signal in our design? What implications does this have for synchronization?

R is the ready signal sent by the memory in Patt and Patel. It is 1 whenever memory is done reading or writing, i.e., finished its process and is ready to perform a new task. We do not have this signal in our design because we are using a SRAM. We compensate by having 3 wait states for our SRAM to finish its read/write. This is because we know it takes 3 cycles for the memory to done processing. Therefore, by having 3 wait states, we know for a fact that the data would be available to us in the third state. Hence, we avoid any synchronization error with our clock as the processing time for memory is fixed.

Conclusion:


Our design for both weeks was fully functional. However, we had two major problems while we were trying to debug week 2 of the lab. Firstly, we noticed that in quite a few places we had forgotten to set LD.REG for register file to high whenever we were trying to set a particular register to some value. The other mistake we did was using one always comb block for the entire data path. This was quite difficult to debug as in theory it should have worked as everything in the always_comb is supposed to have sequentially. However, in practice, things don't exactly work that way, and thus we learned we should always try to use multiple always comb blocks for different parts of the data path whenever possible.

There was nothing particularly ambiguous about this lab other than writing the test bench. I feel like writing good test benches is something that has not been taught to us and is extremely important to learn to be successful in this course. So, something that could be improved is giving better resources teaching us how to write test benches. Something that the lab did well was the

level of description and resources provided to help complete the lab (such as the lab manual, the control signal, etc).

Extra Credit:

XOR Test:

 

As we can see, the clock is 0 at PC = x1A. We have XOR'ed the values x01 and x02 which should give us x03. As we can see from the screenshot, it takes 9 clock cycles to compute the final answer. Hence, we get the answer finally at PC x23.

Cycles: 11

Instructions: 9

Instructions per seconds: $(9 * 50,000,000) / 11 = 40.909 \text{ MIPS}$.

Multiplier Test:

 


Figure 16. Begin of Multiply

 


Figure 17. End of Multiply

As we can see, the clock is 0 at PC = x3A. We have multiplied the values x01 and x02 which should give us x03. As we can see from the screenshot, it takes 99 clock cycles to compute the final answer. Hence, we get the answer finally at PC x48.

Cycles: 99

Instructions: 98

Instructions per seconds: $(98 * 50,000,000) / 99 = 49.494 \text{ MIPS}$.

Sort Test:

Type	Alias	Name	-2023alt2022	-2	-1	0	1	2	3	4
IO		SW[9..0]								
R		...emory_subsystem hex_data[15..0]								
R		...0 reg_16:PC_REG Data_Out[0..15]		0067h	0068h	0077h	0078h	0079h	007Ah	

Figure 18. Begin of Sort

Type	Alias	Name	0 gmi	1846	1854	1861	1866	1871	1877	1884	1892	1899	1907	1916
IO		SW[9..0]	-407alt4070	1624	1632	1640	1648	1656	1664	1672	1680	1688	1696	1704
R		...emory_subsystem hex_data[15..0]		002h							0001h	0003h	0007h	
R		...0 reg_16:PC_REG Data_Out[0..15]				005Fh								

Figure 19. End of Sorted

As we can see, the clock is 0 at PC = x77. We have sorted the values which were already present in the memory. As we can see from the screenshot, it takes 1651 clock cycles to compute the sorted answer. Hence, we get the answer finally at PC x5F.

Cycles: 1651

Instructions: 1638

Instructions per seconds: $(1638 * 50,000,000) / 1651 = 49.606 \text{ MIPS}$.